

ARITHMETIC AND LOGIC UNIT

Mahdi Nazm Bojnordi

Assistant Professor

School of Computing

University of Utah

Overview

- This lecture
 - ▣ How to design ALU
 - Design rules
 - Common logic blocks
 - Designing multi-function blocks


Design Rules

- Any Boolean function can be represented by a **truth table** and **sum of products** (two gate levels)

A	B	C	E
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Sum of Products

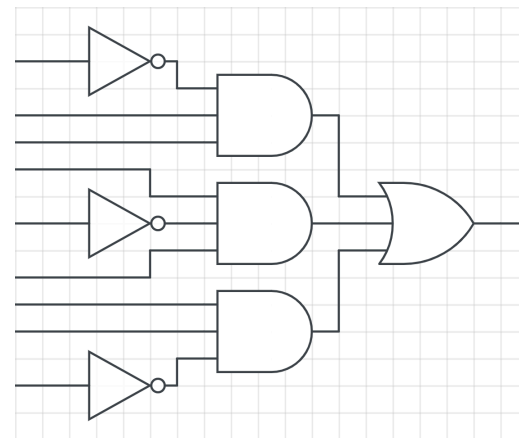
$$E = (\bar{A}.B.C) + (A.\bar{B}.C) + (A.B.\bar{C})$$




Common Logic Blocks

- An n-input **decoder** takes n inputs, based on which only one out of 2^n outputs is activated

2-to-4

 


3-to-8 (using two 1-to-4 units)

 


Common Logic Blocks

- An n-input **decoder** takes n inputs, based on which only one out of 2^n outputs is activated

2-to-4

 


3-to-8 (using two 1-to-4 units)

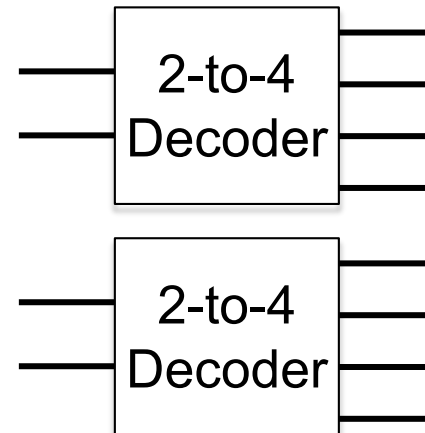


Common Logic Blocks

- A **multiplexer (or selector)** reflects one of n inputs on the output depending on the value of the select bits

2-to-1

 


4-to-1 (using three 2-to-1 units)

 


Common Logic Blocks

 
- A **full adder** generates the sum (S) and carry (Cout) for inputs A, B, and Cin.



Example Ckt 1:

 


Example Ckt 2:

 


Multi-Function Blocks

 - A 1-bit ALU with ADD, OR, and AND operations
 - ▣ A multiplexer selects between the operations




Multibit ALU

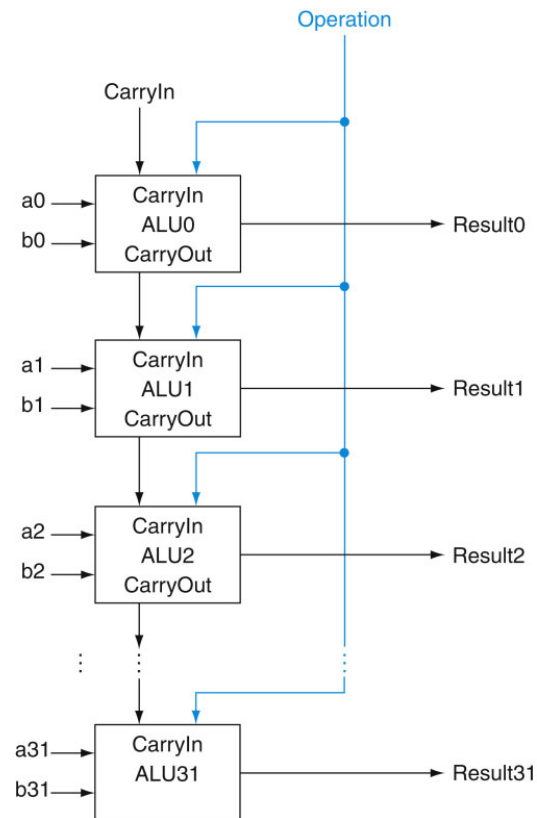- 1-bit ALUs are connected “in series” with the carry-out of 1 box going into the carry-in of the next box




Incorporating Subtraction

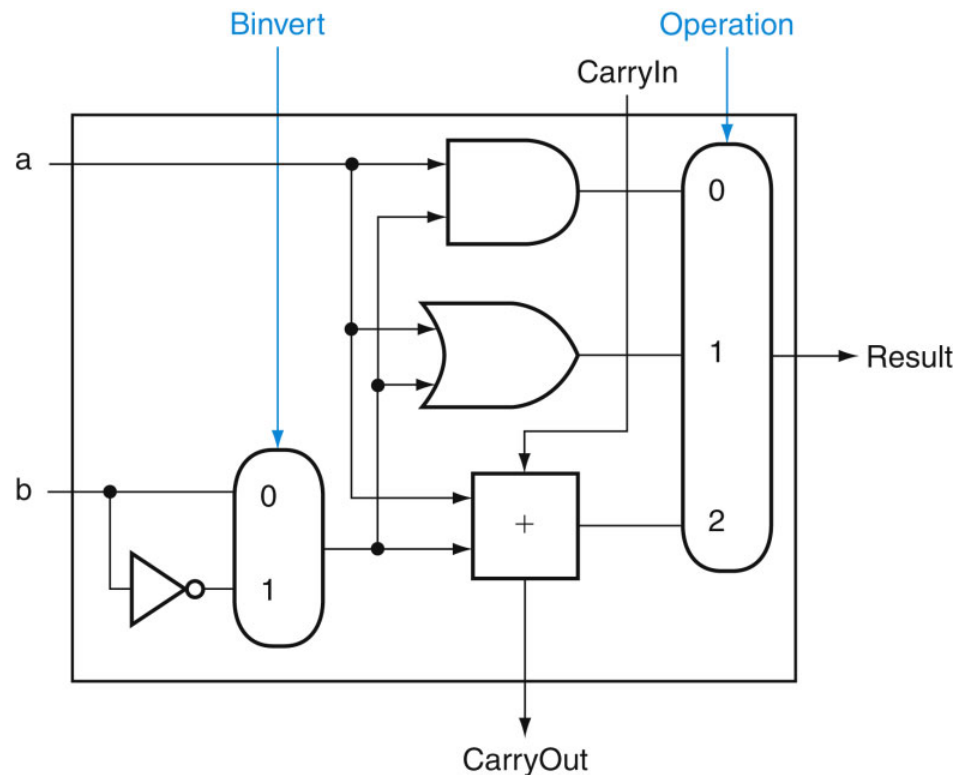- Must invert bits of B and add a 1
 - ▣ Include an inverter **CarryIn** for the first bit is 1
- The **CarryIn** signal (for the first bit) can be the same as the **Binvert** signal



Incorporating NAND and NOR

 
- Must invert bits of A and B to realize NAND and NOR
 - ▣ Recall DeMorgan's Laws



Incorporating Comparison

□ For example: the `slt` instruction

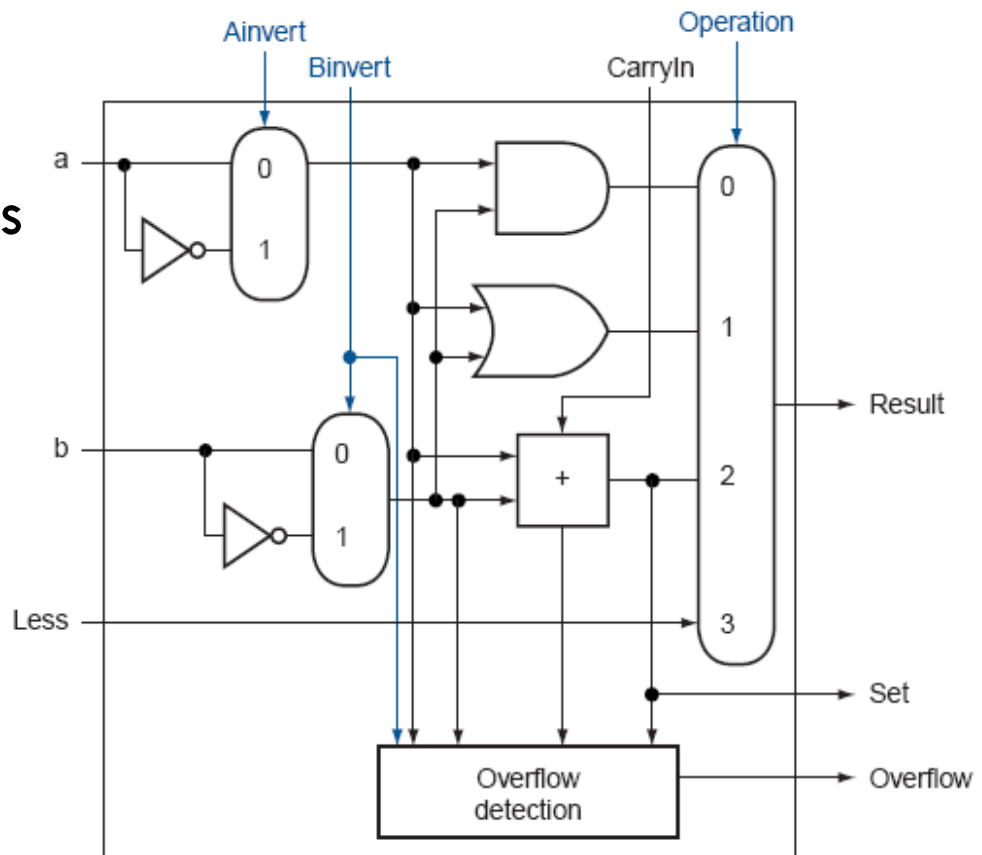- Perform $a - b$ and check the sign
- New signal (Less) that is zero for ALU boxes 1-31
- The 31st box has a unit to detect overflow and sign – the sign bit serves as the Less signal for the 0th box




Incorporating Comparison

□ For example: the **beq** instruction

▣ Perform $a - b$ and confirm that the result is all zero's

▣ What about **bne**?

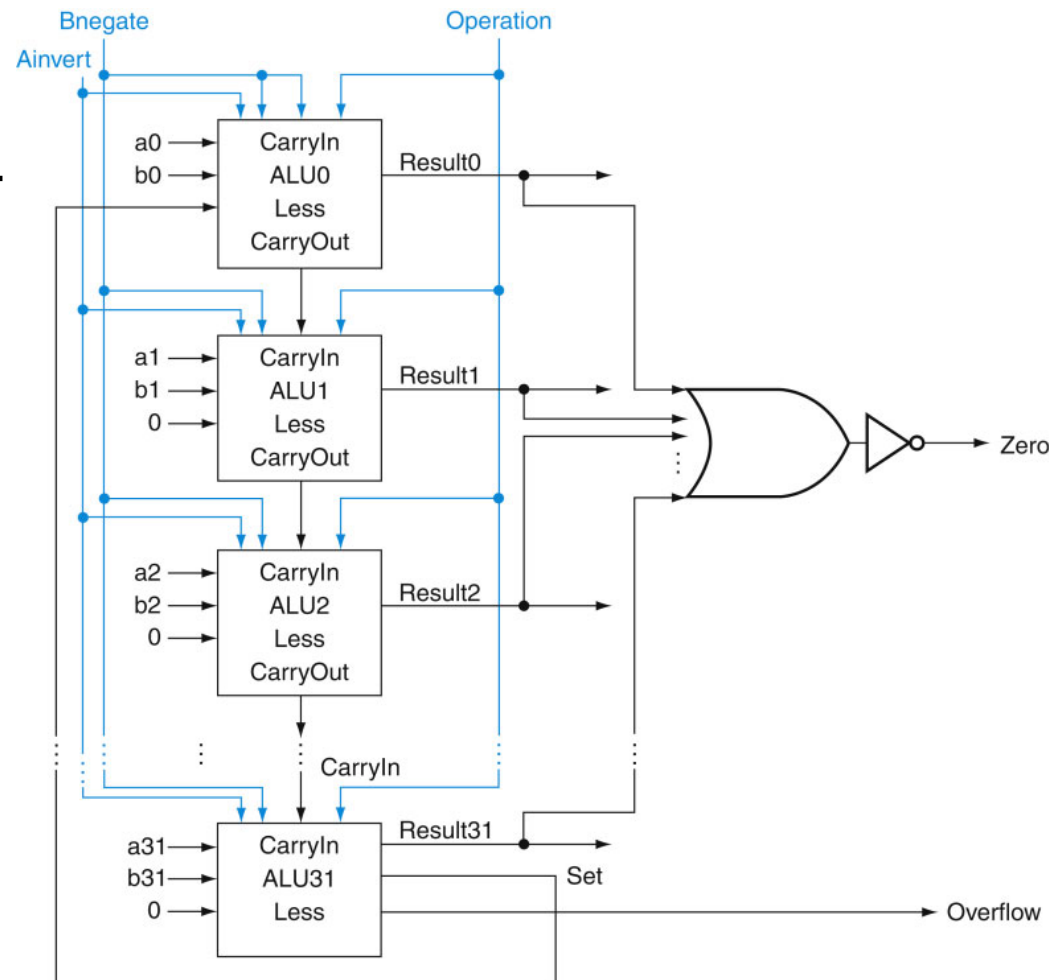▣ Control lines determine what operations to be done.



Incorporating Comparison


□ For example: the **beq** instruction

▣ Perform $a - b$ and confirm that the result is all zero's

▣ **What about bne?**


▣ Control lines determine what operations to be done.

	Ai	Bn	Op
AND	0	0	00
OR	0	0	01
Add	0	0	10
Sub	0	1	10
SLT	0	1	11
NOR	1	1	00

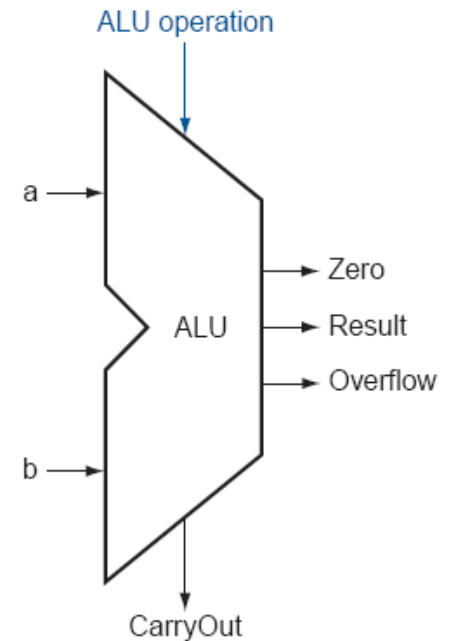

Carry Ripple Adder

 - Simplest design by cascading 1-bit boxes
 - ▣ Each 1-bit box sequentially implements AND and OR
 - ▣ Critical path: the total delay is the time to go through 64 gates
- How to make a 32-bit addition faster?



Carry Ripple Adder

- Simplest design by cascading 1-bit boxes
 - ▣ Each 1-bit box sequentially implements AND and OR
 - ▣ Critical path: the total delay is the time to go through 64 gates
- How to make a 32-bit addition faster?
- **Recall:** any logic equation can be expressed as the sum of products (only 2 gate levels!)
 - ▣ Challenges: many parallel gates with very large inputs
 - ▣ **Solution:** we'll find a compromise